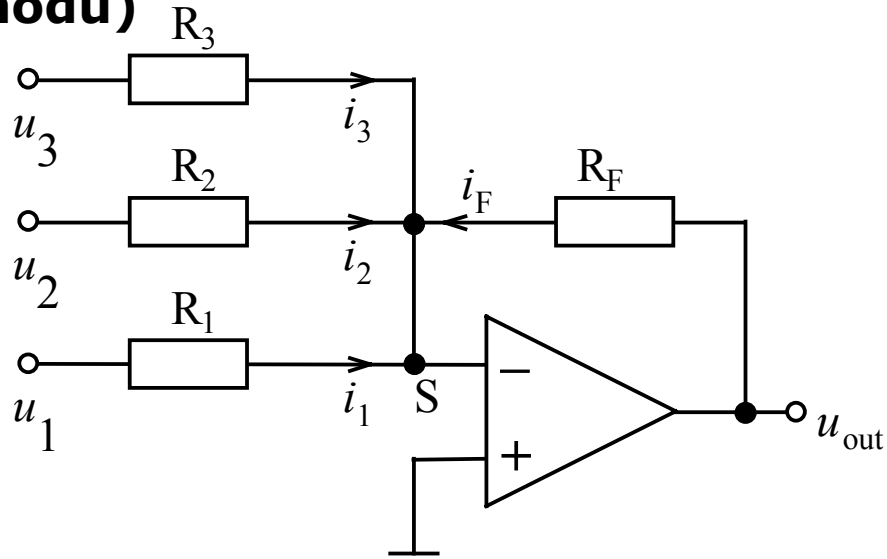


Linearna vezja z OP

➤ **seštevalnik (na – vohu)**



$$i_1 + i_2 + \dots + i_3 + i_F = 0$$


$$\frac{u_1}{R_1} + \frac{u_2}{R_2} + \dots + \frac{u_3}{R_3} + \frac{u_{out}}{R_F} = 0$$

$$-u_{out} = \frac{R_F}{R_1} \cdot u_1 + \frac{R_F}{R_2} \cdot u_2 + \dots + \frac{R_F}{R_3} \cdot u_3$$

$$u_{out} = -\sum_{i=1}^n u_i$$


Linearna vezja z OP

➤ seštevalnik (na + vohodu)

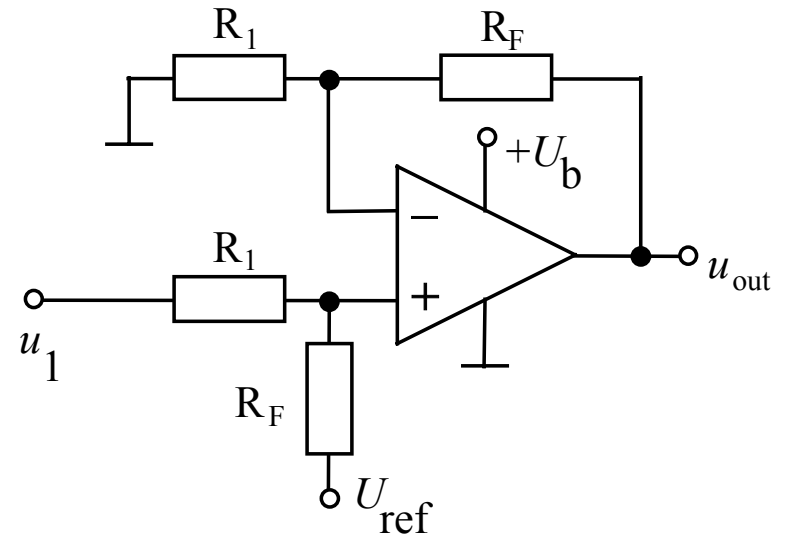

Linearna vezja z OP

➤ odštevalnik

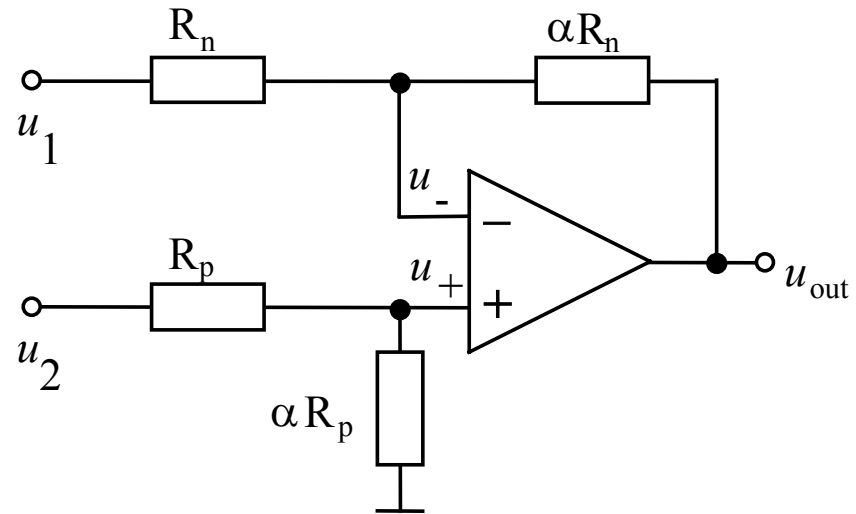


$$\frac{u_1 - u_-}{R_n} + \frac{u_{out} - u_-}{\alpha R_n} = 0 \quad \text{in s tem} \quad \alpha u_1 + u_{out} = u_-(\alpha + 1)$$

$$u_+ = u_2 \frac{\alpha}{\alpha + 1}$$

Ker velja $u_p = u_n$, dobimo $u_{out} = \alpha(u_2 - u_1)$

Linearna vezja z OP

➤ integrator

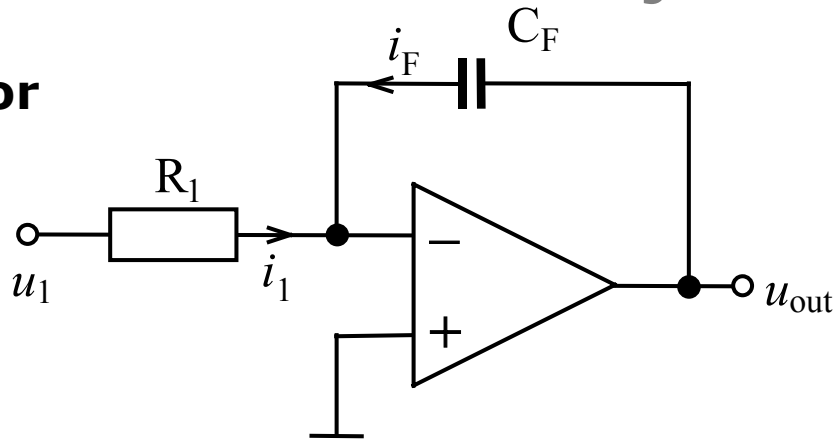


$$i_1 + i_F = 0$$

$$\frac{u_1}{R_1} + C_F \frac{du_{out}}{dt} = 0$$

$$du_{out} = -\frac{1}{R_1 C_F} u_1 dt$$


$$u_{out}(t) = -\frac{1}{T_I} \int_0^t u_1(t) dt + U_{out}(0)$$
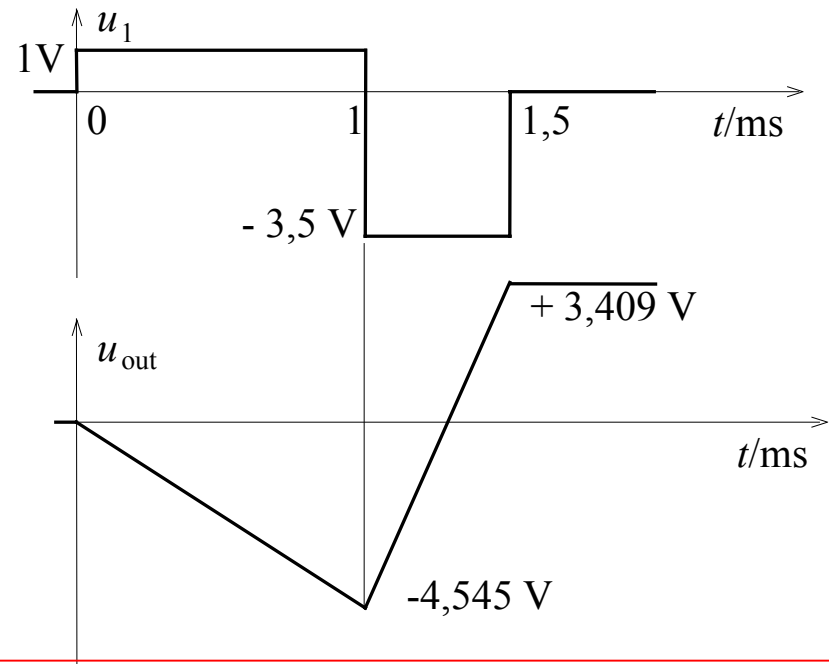
$$R_1 = 10 \text{ k}\Omega \text{ in } C_F = 22 \text{ nF}$$



Linearna vezja z OP

➤ **integrator**


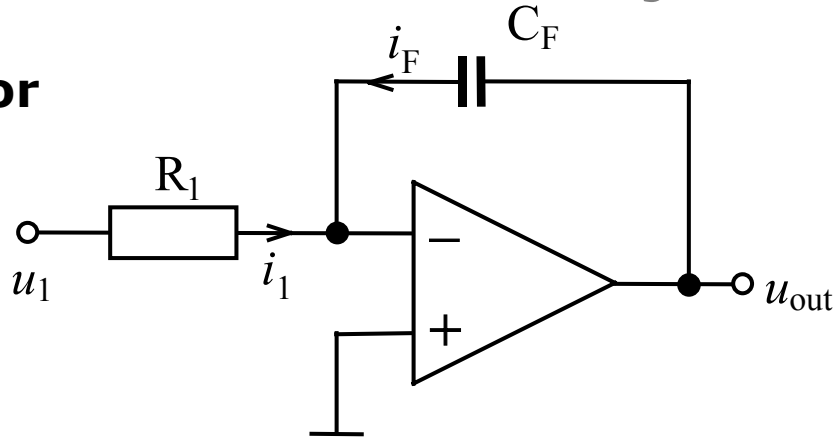


$$I_1 + I_F = 0$$

$$\frac{U_1}{R_1} + j\omega C_F \cdot U_{out} = 0$$

$$U_{out}(j\omega) = -\frac{1}{j\omega R_1 C_F} U_1(j\omega)$$
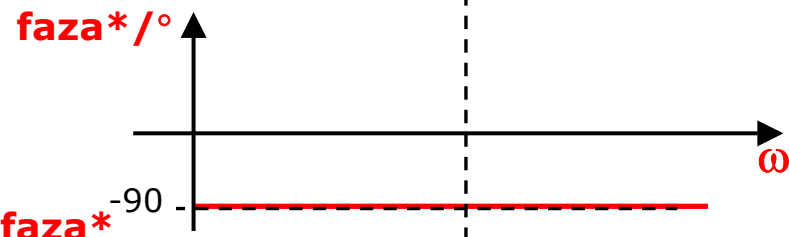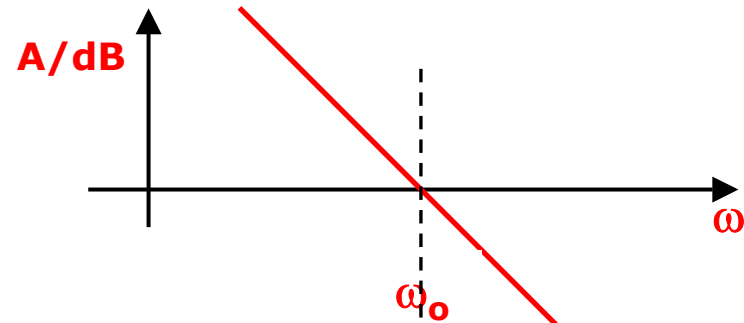
$$F(p) = \frac{U_{out}(p)}{U_1(p)} = -\frac{1}{T_I p}$$




faza = 180 ° + faza*

Linearna vezja z OP

➤ integrator razlike

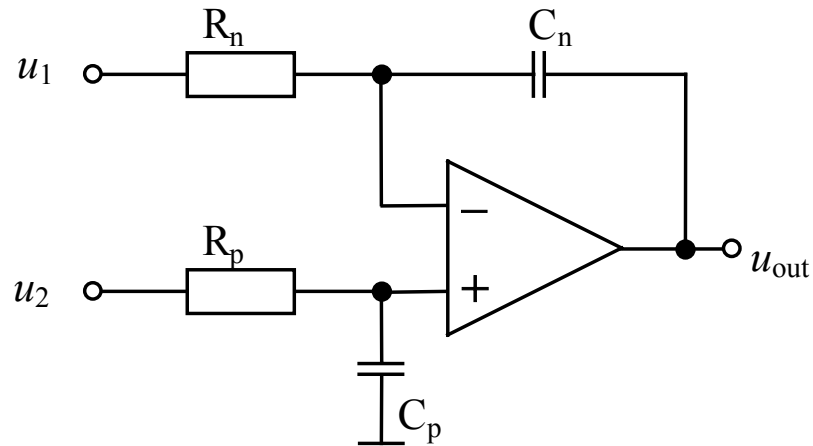Izpelji izraz za izh.napetost ob pogoju: $R_n C_n = R_p C_p = T_I$,




rešitev

rešitev

Linearna vezja z OP

➤ diferenciator

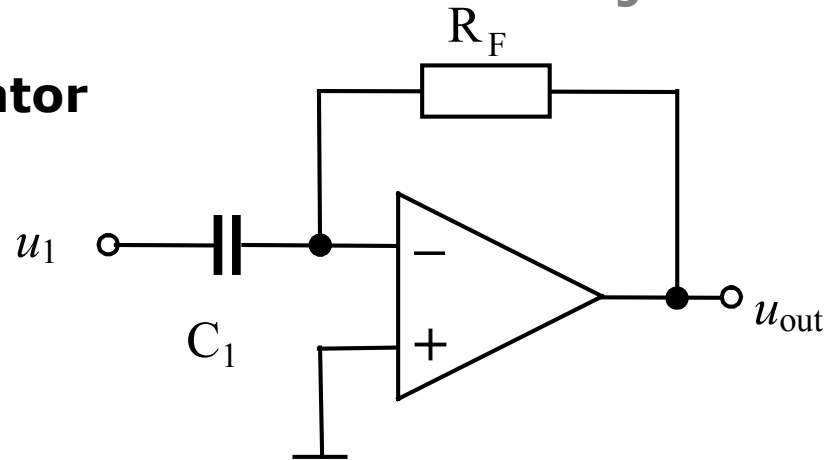


$$i_1 + i_F = 0$$

rešitev

Linearna vezja z OP

➤diferenciator

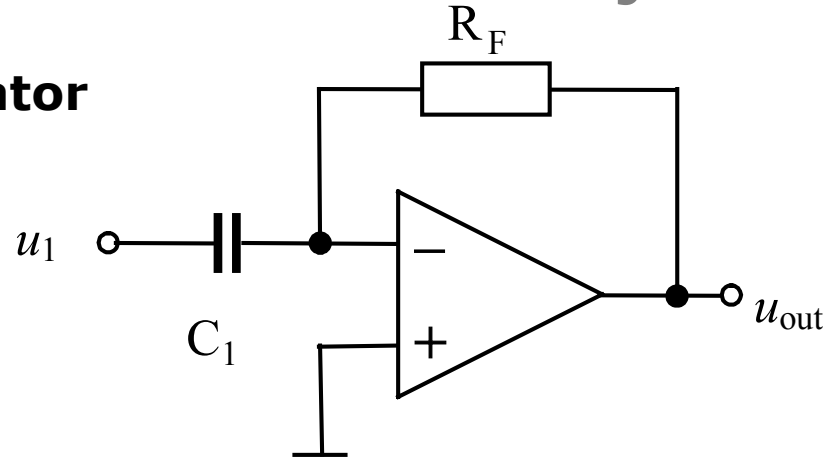


$$I_1 + I_F = 0$$

$$\frac{U_1(j\omega)}{\frac{1}{j\omega C_1}} + \frac{U_{out}(j\omega)}{R_F} = 0$$

$$U_{out}(j\omega) = -j\omega R_F C_1 U_1(j\omega) = -j\omega T_D U_1(j\omega)$$

$$F(p) = \frac{U_{out}}{U_1} = -pT_D$$

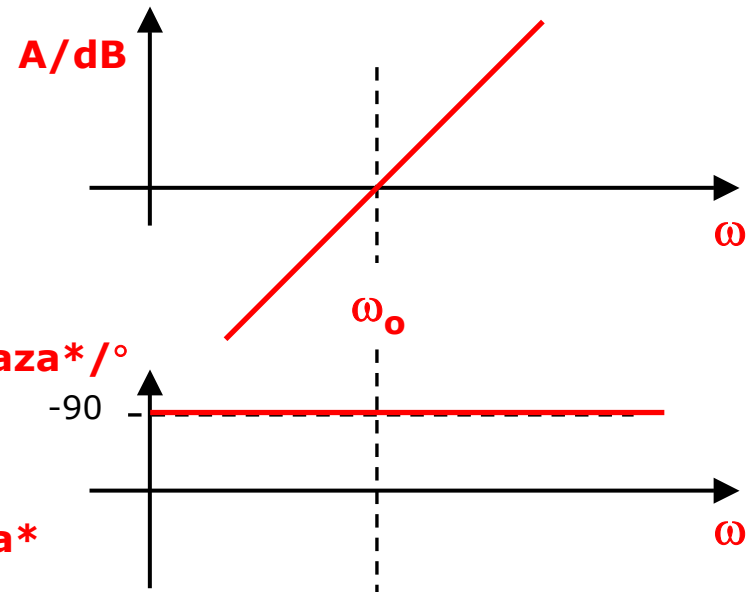

faza = 180 °+faza*

Linearna vezja z OP

➤diferenciator


1) analiza vezja brez kondenzatorja C_F

$$\frac{U_1(j\omega)}{R_1 + \frac{1}{j\omega C_1}} + \frac{U_{out}(j\omega)}{R_F} = 0 \quad \text{od tu: } U_{out} = -\frac{j\omega R_F C_1}{1 + j\omega R_1 C_1} U_1$$

če vstavimo $T_0 = R_1 C_1$

$$U_{out}(j\omega) = -\frac{R_F}{R_1} \cdot \frac{j\omega T_0}{1 + j\omega T_0} \cdot U_1(j\omega) \quad \longrightarrow \quad F(p) = \frac{U_{out}(p)}{U_1(p)} = -\frac{R_F}{R_1} \cdot \frac{pT_0}{pT_0 + 1}$$



diferencialni člen 1.reda (DT_1)

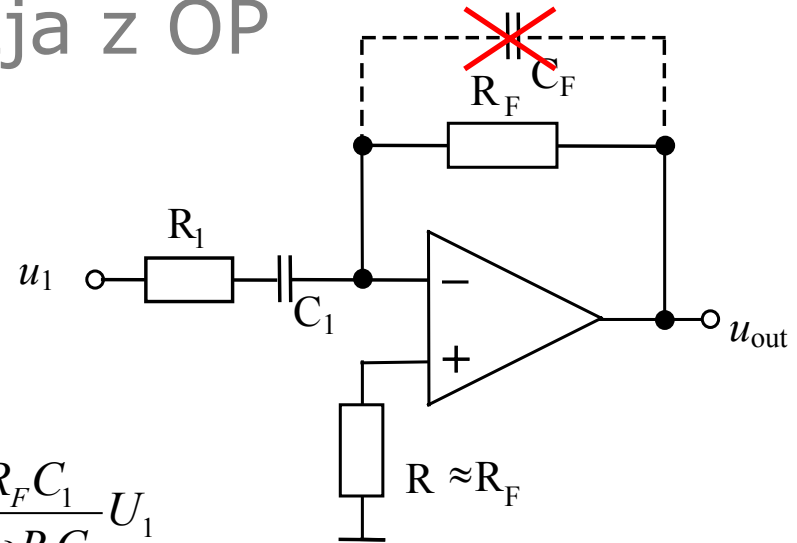

Linearna vezja z OP

diferencialni člen 1.reda (DT_1)
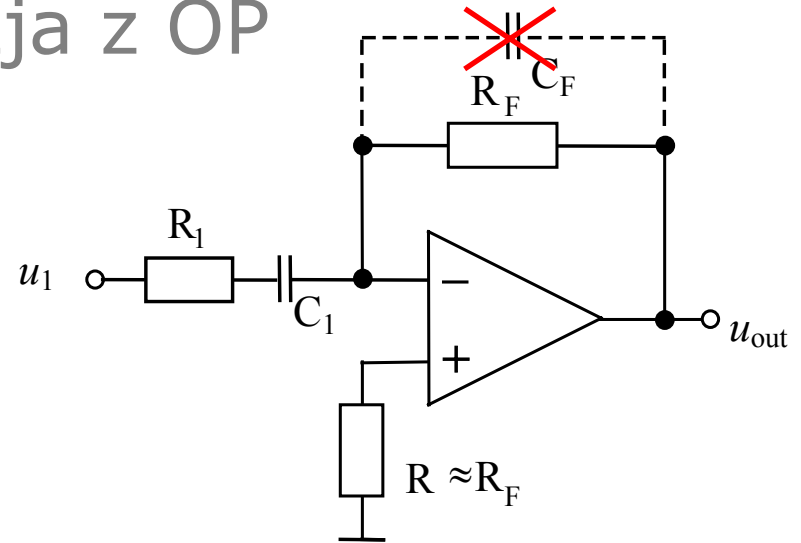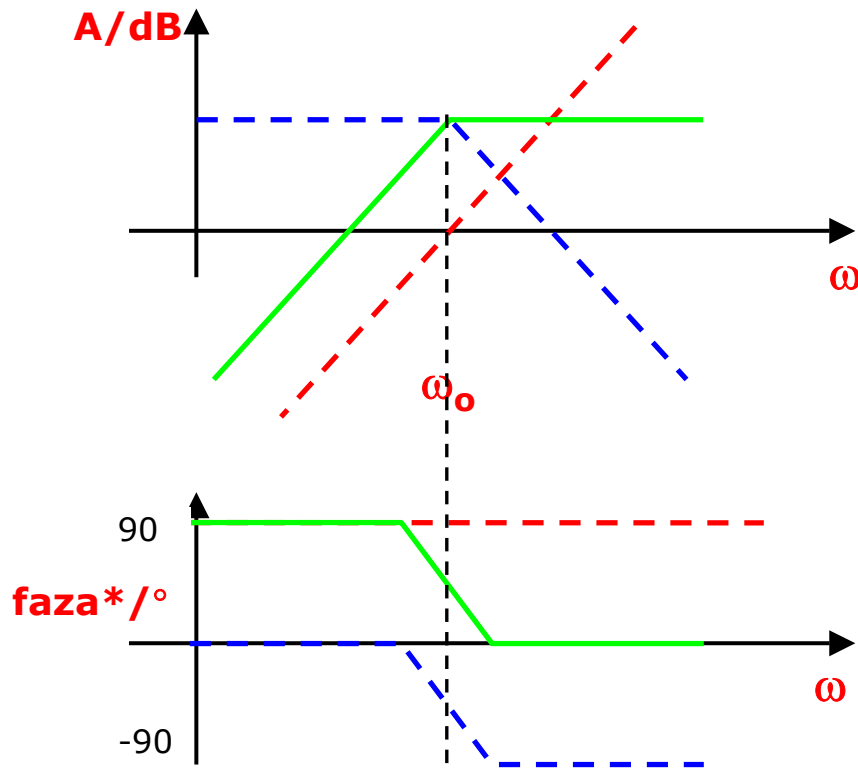
$$U_{out}(j\omega) = -\frac{R_F}{R_1} \cdot \frac{j\omega T_0}{1 + j\omega T_0} \cdot U_1(j\omega)$$




faza = 180 ° + faza*

Linearna vezja z OP

➤ diferenciator

2) analiza vezja s kondenzatorjem C_F

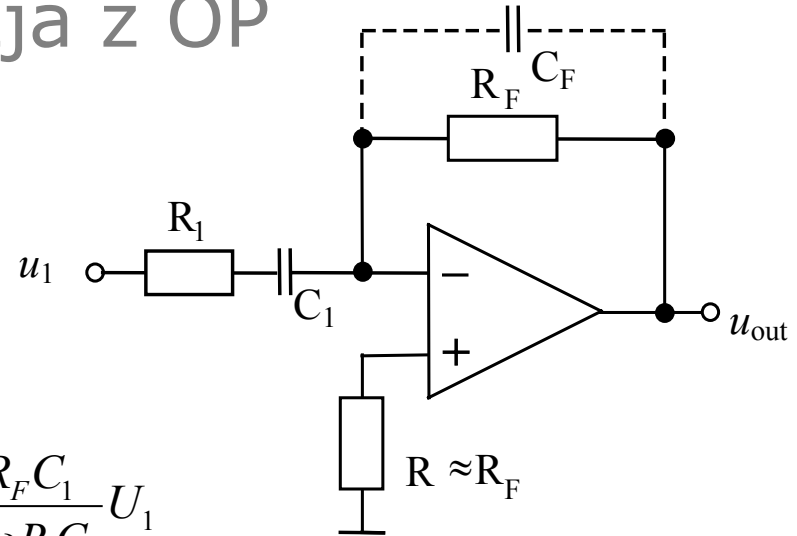

$$\frac{U_1(j\omega)}{R_1 + \frac{1}{j\omega C_1}} + \frac{U_{out}(j\omega)}{R_F} = 0 \quad \text{od tu: } U_{out} = -\frac{j\omega R_F C_1}{1 + j\omega R_1 C_1} U_1$$

$$U_{out}(j\omega) = -\frac{R_F}{R_1} \cdot \frac{j\omega T_0}{(1 + j\omega T_0)(1 + j\omega T_1)} U_1(j\omega), \text{ kjer je } T_1 = R_F C_F, T_0 = R_1 C_1$$




$$\Rightarrow F(p) = -\frac{R_F}{R_1} \cdot \frac{pT_0}{(1 + pT_0)(1 + pT_1)}$$

diferencialni člen 2.reda (DT₂)

Linearna vezja z OP

diferencialni člen 2.reda (DT₂)

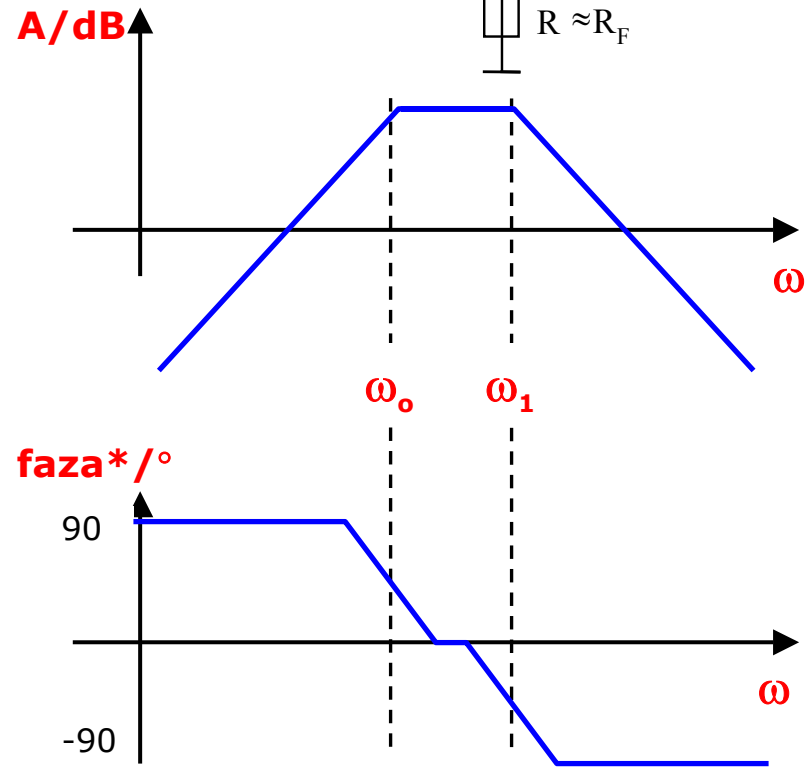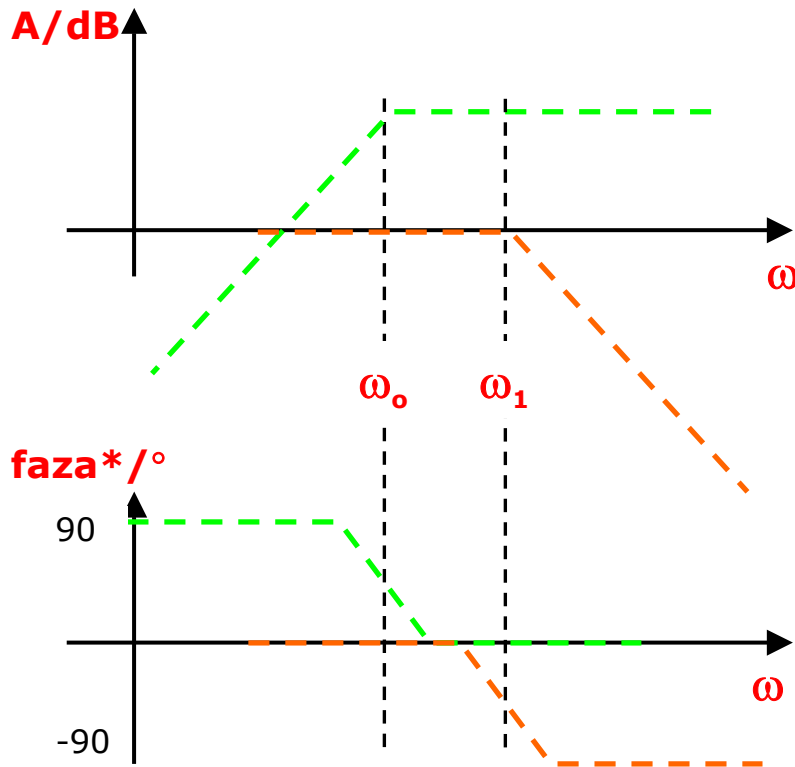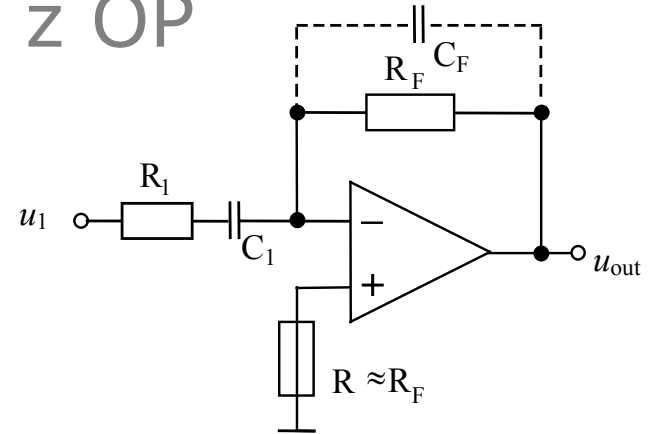
$$U_{out}(j\omega) = -\frac{R_F}{R_1} \cdot \frac{j\omega T_0}{(1+j\omega T_0)(1+j\omega T_1)} U_1(j\omega)$$



faza = 180° + faza*

Nelinearna vezja z OP

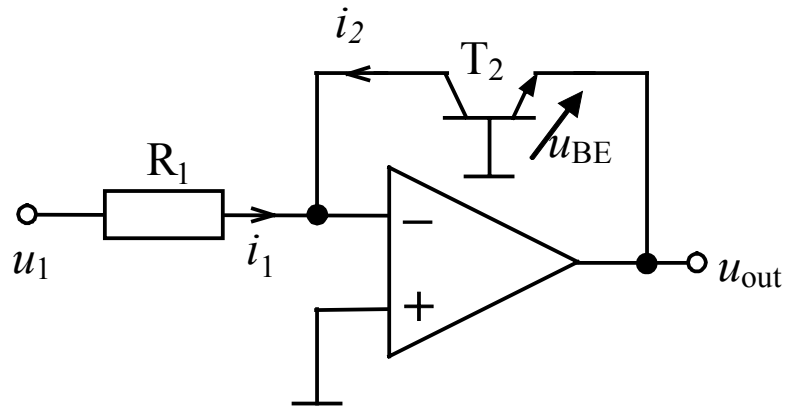➤ logaritemski ojačevalnik - osnova analognega množenja



$$i_C \approx I_{ES} \left(e^{\frac{u_{BE}}{U_T}} - 1 \right) - I_{CS} \left(e^{\frac{u_{BC}}{U_T}} - 1 \right)$$

$u_{BC} = 0$


obratovanje pod napetostjo kolena pn spoja!

$$u_{OUT} = -U_T \cdot \ln \left[\frac{u_1}{I_{ES} \cdot R_1} + 1 \right] \quad \Rightarrow \quad u_{OUT} = -U_T \cdot \ln \left[\frac{u_1}{I_{ES} \cdot R_1} \right]$$

Nelinearna vezja z OP

➤ množilnik
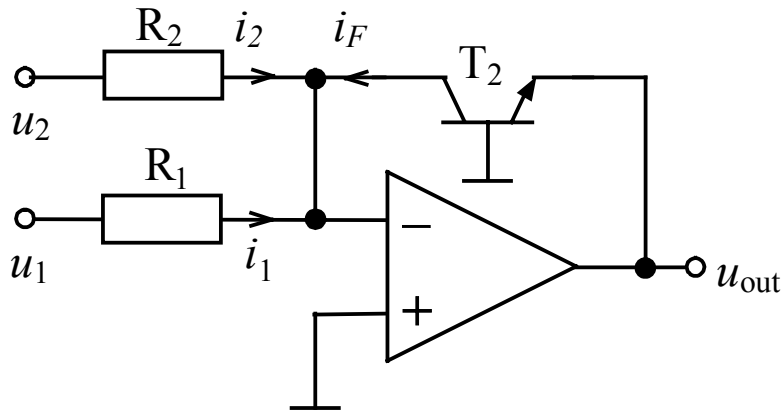
$$\underline{\ln u_1 + \ln u_2 = \ln(u_1 \cdot u_2)}$$




$$u_{OUT} = -U_T \cdot \left[\ln \left[\frac{u_1}{I_{ES} \cdot R_1} \right] + \ln \left[\frac{u_2}{I_{ES} \cdot R_2} \right] \right]$$



**izraz je treba
antilogaritmirati**

Nelinearna vezja z OP

➤ eksponencialni ojačevalnik

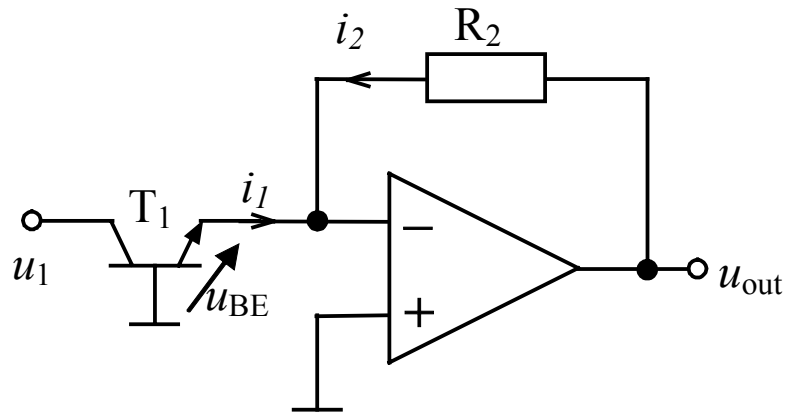

$$i_C \approx I_{ES} \left(e^{\frac{u_{BE}}{U_T}} - 1 \right) - I_{CS} \left(e^{\frac{u_{BC}}{U_T}} - 1 \right)$$

$u_{BE} = 0$

obratovanje pod napetostjo kolena pn spoja!

$$u_{OUT} = I_{CS} R_2 \left[e^{\frac{-u_1}{U_T}} - 1 \right] \quad \Rightarrow$$

$$u_{OUT} = I_{CS} R_2 e^{\frac{-u_1}{U_T}}$$